

LIST OF FIGURES

Figure	Page
1.1. Cross-sectional view of one pole of a 4 pole IPM machine	4
1.2. Schematic diagram of an IPM generator feeding an RL load with shunt capacitors placed at the terminals of the IPM	4
1.3 Schematic diagram of an IPM generator feeding a 3-phase full bridge rectifier resistive load	9
1.4. Schematic diagram of an IPM generator feeding a rectifier-boost-resistive load	9
1.5. Schematic diagram of an IPM generator feeding a rectifier-buck-resistive load ..	10
1.6. Schematic diagram of an IPM generator feeding an induction motor	10
2.1. Model of a brushless PM synchronous machine	14
2.2. Schematic diagram representing the steady state q and d axis voltage equations of a PM machine	24
2.3. Schematic diagram of dc test used to determine stator resistance	26
2.4. Measured line to neutral rms terminal generator voltage vs air gap voltage for no load condition for machine connected in high and low voltage stator connections	29
2.5. Measured values of q axis inductance vs peak stator current	32
2.6. Measured d axis inductance vs peak stator current	33
2.7. Measured magnetic flux vs peak stator current.	34
2.8. Measured q axis inductance vs peak mutual flux	35
3.1. IPM generator feeding an RL impedance load with capacitive compensation	39

Figure	Page
3.2. D Q equivalent circuit of IPM machine connected to an RLC load	39
3.3. Equivalent circuit of dq representation of IPM machine connected to a resistive load with shunt capacitive compensation	46
3.4. Equivalent circuit of IPM machine feeding a resistive load	49
3.5. Measured and calculated line to neutral generator voltage vs load power output for various generator frequencies	52
3.6. Measured and calculated generator line current vs output power for various frequencies	53
3.7. Measured and calculated load voltage vs load resistance	54
3.8. Measured and calculated output power vs load resistance for various frequencies	55
3.9. Measured and calculated line to line generator voltage vs stator current for various frequencies	56
3.10. Measured and calculated line to neutral generator voltage vs output power for PM machine with capacitor compensation	57
3.11. Measured and calculated generator line current vs output power for PM machine with capacitor compensation	58
3.12. Measured and calculated line to neutral generator voltage vs per phase load resistance for shunt capacitor scheme	59
3.13. Measured and calculated output power vs load resistance for capacitor compensation scheme	60
3.14. Measured and calculated stator current vs line to neutral generator voltage for capacitor compensation scheme	61
3.15. Measured and simulated line to line voltage waveforms for the generator feeding a 22 Ω resistive load. Rotor speed=1350 rpm. Measured waveform scale: voltage:50v/div, time 5ms/div.	63

Figure	Page
3.16. Measured and simulated generator currents waveforms for a 22 Ω load. Rotor speed=1350 rpm. Measured waveform scale: current: 1A/div, time 5ms/div...	64
3.17. Measured and simulated load currents for a 22 Ω load. Rotor speed=1350 rpm. Measured waveform scale: current: 1A/div, time 5ms/div.....	64
3.18. Measured and simulated waveforms of the line to line voltage for a 205 Ω load. Rotor speed = 1350 rpm. Measured waveform scale: voltage:50V/div, time 5ms/div	65
3.19. Measured and simulated waveforms of generator current for a 205 Ω load. Rotor speed=1350 rpm. Measured waveform scale: current: 200 mA/div, time 5ms/div.....	66
3.20. Measured and simulated waveforms of load current for a 205 Ω load. Rotor speed=1350 rpm. Measured waveform scale: current:100 mA/div, time 5ms/div.....	66
4.1. Schematic diagram of IPM-Rectifier feeding an impedance load.....	70
4.2. Schematic diagram of 3 phase full bridge rectifier.....	70
4.3. Measured and calculated line to neutral voltage vs output power for IPM machine.	79
4.4. Measured and calculated load power vs load resistance for IPM feeding a rectifier-resistive load.....	80
4.5. Measured and calculated load voltage vs generator current for IPM feeding a rectifier-resistive load.....	81
4.6. Measured and calculated load voltage vs generator output power.....	82
4.7. Measured power loss in the rectifier vs the load resistance.....	83
4.8. Resistive-Inductive model of a UI diode.....	85
4.9. Simulink model of a UI diode.....	85
4.10. Simulink representation of a UI diode.....	85

Figure	Page
4.11. Simulink model of an IU diode.....	87
4.12. Simulink representation of an IU diode	87
4.13. Simulink models of (a) a UI Inductor and (b) an IU capacitor.....	87
4.14. Simulink models of (a) an IU inductor and (b) a UI capacitor	89
4.15. Schematic diagram of full bridge rectifier with filter feeding a resistive load	89
4.16. Simulink model of 3-phase full bridge rectifier with filter feeding a resistive load	90
4.17. Simulink model of filter and resistive load	90
4.18. Load voltage vs time for ideal voltage source feeding rectifier	91
4.19. Simulated waveform of capacitor current vs time for ideal voltage source feeding a rectifier.....	92
4.20. Simulated waveform of input current into the rectifier vs time.....	93
4.21. Simulated waveform of current flowing through the inductor filter for ideal voltage source feeding a rectifier	94
4.22. Measured and simulated line to line voltage waveforms for the generator feeding a rectifier-resistive 22 Ω resistive load. Rotor speed=1350 rpm. Measured waveform scale: voltage:50v/div, time 5ms/div.	96
4.23. Measured and simulated generator currents waveforms for a 22 Ω load. Rotor speed=1350 rpm. Measured waveform scale: current 2A/div, time 5ms/div.	97
4.24. Measured and simulated rectifier input currents for a 22 Ω rectifier-resistive load. Rotor speed=1350 rpm. Measured waveform scale: current: 2A/div, time: 5ms/div.....	97
4.25. Measured and simulated capacitor currents for a 22 Ω rectifier-resistive load. Rotor speed=1350 rpm. Measured waveform scale: current:1A/div, time 5ms/div.....	98

Figure	Page
4.26. Measured and simulated waveforms of the line to line voltage for a 132 ohm rectifier-resistive load. Rotor speed = 1350 rpm. Measured waveform scale: voltage:50v/div, time 5ms/div.	99
4.27. Measured and simulated waveforms of the generator line current for a 132 ohm rectifier-resistive load. Rotor speed = 1350 rpm. Measured waveform scale: current:500mA/div, time 5ms/div.	99
4.28. Measured and simulated waveforms of the input rectifier current for a 132 ohm rectifier-resistive load. Rotor speed = 1350 rpm. Measured waveform scale: current:500 mA/div, time 5ms/div.	100
4.28. Measured and simulated waveforms of the a.c. capacitor current for a 132 ohm rectifier-resistive load. Rotor speed = 1350 rpm. Measured waveform scale: current: 500 mA/div, time 5ms/div.	101
4.30. Measured and simulated waveforms of the line to line generator voltage for a 132 ohm rectifier-resistive load. Rotor speed = 1350 rpm. Measured waveform scale: voltage: 50 V/div, time 5ms/div.	102
4.31. Measured and simulated waveforms of the generator current for a 132 ohm rectifier-resistive load. Rotor speed = 1350 rpm. Measured waveform scale: current: 1A/div, time 5ms/div.	102
4.32. Fast Fourier transform of measured and simulated waveforms of the generator line to line voltage for a 132 ohm rectifier-resistive load. Rotor speed = 1350 rpm.	103
4.33. Fast Fourier transform of measured and simulated waveforms of the generator line current for a 132 ohm rectifier-resistive load. Rotor speed = 1350 rpm.	104
4.34. Measured and simulated waveforms of the load voltage for a 132 ohm rectifier-resistive load. Rotor speed = 1350 rpm. Measured waveform scale: voltage: 5V/div, time 200ms/div.	105
5.1. Basic dc-dc converter and associated voltage output	107
5.2. Dc-dc (buck) converter with low pass filter	108

Figure	Page
5.3. Control signal and saw tooth voltage waveforms and switching signal sent to turn switch on and off	109
5.4. Schematic diagram of comparators and op-amp used to control the signal of a converter	109

Figure	Page
5.19. Plot of converter efficiency vs duty ratio for the IPM feeding a rectifier-buck-resistive load topology	135
5.20 Measured power loss vs duty ratio for the IPM feeding a rectifier-buck resistive load	136
5.21. Simulink model of a UI transistor.....	138
5.22. Simulink model of an IU transistor.....	138
5.23. Simulink symbolic representations of (a) a UI transistor and (b) an IU transistor	139
5.24. Generation of switching scheme for transistor. (a) a dc signal superimposed upon a triangle wave, (b) signal sent to transistor	139
5.25. Measured and simulated line to line voltage waveforms for the generator feeding a rectifier-buck-resistive 10 Ω resistive load. Rotor speed=900 rpm. Measured waveform scale: voltage:50v/div, time 10ms/div.	141
5.26. Measured and simulated generator current waveforms for the generator feeding a rectifier-buck-resistive 10 Ω resistive load. Rotor speed=900 rpm. Measured waveform scale: current: 1A/div, time 5ms/div.	142
5.27. Measured and simulated buck inductor current waveforms for the generator feeding a rectifier-buck-resistive 10 Ω resistive load. Rotor speed=900 rpm. Measured waveform scale: current: .1A/div, time .2ms/div	142
5.28. Measured and simulated buck transistor current waveforms for the generator feeding a rectifier-buck-resistive 10 Ω resistive load. Rotor speed=900 rpm. Measured waveform scale: current: 1A/div, time .2ms/div.....	143
5.29. Measured and simulated generator line to line voltage waveforms for the generator feeding a rectifier-buck-resistive 10 Ω resistive load. Rotor speed=900 rpm. Measured waveform scale: voltage: 50v/div, time 2ms/div.	144
5.30. Measured and simulated generator line current waveforms for the generator feeding a rectifier-buck-resistive 10 Ω resistive load. Rotor speed=900 rpm. Measured waveform scale: current: .5A/div, time 2ms/div	145

Figure

Page

6.14. Measured and calculated load voltage vs duty ratio for IPM generator feeding a rectifier-boost-resistive load	170
6.15. Measured power loss of rectifier-boost system vs the duty ratio	171
6.16(a). Measured converter efficiency vs duty ratio for IPM generator feeding rectifier-boost-resistive load	172
6.16(b). Measured and calculated rectifier-boost effective resistance vs duty ratio	174
6.17. Measured and simulated line to line voltage waveforms for the generator feeding a rectifier-boost-resistive 77Ω resistive load. Rotor speed=900 rpm. Measured waveform scale: voltage:20v/div, time 10ms/div.	176
6.18. Measured and simulated generator current waveforms for the generator feeding a rectifier-boost-resistive 77Ω resistive load. Rotor speed=900 rpm. Measured waveform scale: current: 2A/div, time 10ms/div.....	176
6.19. Measured and simulated boost inductor current waveforms for the generator feeding a rectifier-boost-resistive 77Ω resistive load. Rotor speed=900 rpm. Measured waveform scale: current: .2A/div, time .2ms/div	177
6.20 Measured and simulated rectifier output current waveforms for the generator feeding a rectifier-boost-resistive 77Ω resistive load. Rotor speed=900 rpm. Measured waveform scale: current: .2A/div, time 2ms/div	177
6.21. Measured and simulated generator line to line voltage waveforms for the	P701=iv=900

Figure	Page
6.24. Measured and simulated rectifier output current waveforms for the generator feeding a rectifier-boost-resistive 77Ω resistive load. Rotor speed=900 rpm. Measured waveform scale: voltage: .2A/div, time 2ms/div	181
7.1. Schematic diagram of IPM machine feeding an induction machine	184
7.2. DQ representation of induction machine with capacitive compensation	184
7.3. Schematic diagram of (a) per phase equivalent circuit, (b) short circuit equivalent circuit, (c) simplified short circuit equivalent circuit, (d) no load equivalent circuit for induction machine	191
7.4. Plot of mutual inductance vs mutual flux linkage for induction motor	195
7.5. Plot of core loss vs mutual flux linkage for induction motor	195
7.6. Plot of rotor resistance vs mutual flux linkage for induction motor	196
7.7. Plot of leakage inductance vs mutual flux linkage for induction motor	196
7.8(a). Measured and calculated load torque of induction motor for three different frequencies	197
7.8(b). Measured and calculated peak generator output voltage vs motor speed for three operating frequencies	198
7.9(a). Measured and calculated peak motor input current vs motor speed	199
7.9(b). Measured and calculated motor input power factor vs motor speed For various operating frequencies.....	200
7.10(a). Measured and calculated motor input power vs motor speed for three operating frequencies.....	201
7.10(b). Measured and calculated peak phase generator voltage vs motor input power	202
7.11. Measured and calculated peak generator voltage vs peak motor input current.....	203

Figure

Page

7.12. Simulated waveforms of (a) generator current, and (b) generator voltage, (c) motor input (stator) current, (d) motor rotor current for IPM-IM topology operating under fan type load	207
7.13. Simulated waveforms of (a) motor speed, (b) load torque, (c) motor electromagnetic torque, (d) electromagnetic and load torque vs motor speed for IPM-IM topology operating under fan type load	208
7.14. Simulated waveforms of (a) generator current, (b) generator voltage, (c) motor input current, and (d) motor rotor current for IPM-IM topology operating under type b load.....	212
7.15. Simulated waveforms of (a) motor speed, (b) load torque, (c) motor electromagnetic torque, (d) electromagnetic and load torque vs motor speed for IPM-IM topology operating under type b load.....	213
7.16. Simulated waveforms of (a) generator current, (b) generator voltage, (c) motor input current, and (d) motor rotor current for IPM-IM topology operating under type b load.....	214
7.17. Simulated waveforms of (a) motor speed, (b) load torque, (c) motor electromagnetic torque, (d) electromagnetic and load torque vs motor speed for IPM-IM topology operating under type b load	215
7.18. Simulated waveforms of (a) generator current, and (b) generator voltage, (c) motor input (stator) current, (d) motor rotor current for IPM-IM topology operating under type c load.....	218
7.19. Simulated waveforms of (a) motor speed, (b) load torque, (c) motor electromagnetic torque, (d) electromagnetic and load torque vs motor speed for IPM-IM topology operating under type c load	219